

# Home Assignment

Rollno  $\rightarrow$  190108022

① ① -ve feedback

Voltage sampling  $\rightarrow$  Current mixing

② Shunt sampling  $\rightarrow$  shunt mixing

③ There is a shunt connection at the output so output resistance  $\downarrow$  by  $(1+AB)$


$$\text{closed loop } R_{out} = \frac{\text{Open loop } R_{out}}{1+AB}$$

There is a shunt connection at ip so  
ip resistance  $\downarrow$  by a factor  $1+AB$

$$CL \text{ to } R_{in} = \frac{OL \text{ } R_{in}}{1+AB}$$

④ At very high  $f_{eq}$   
small signal equivalent

As capacitor get short ckt at High freq

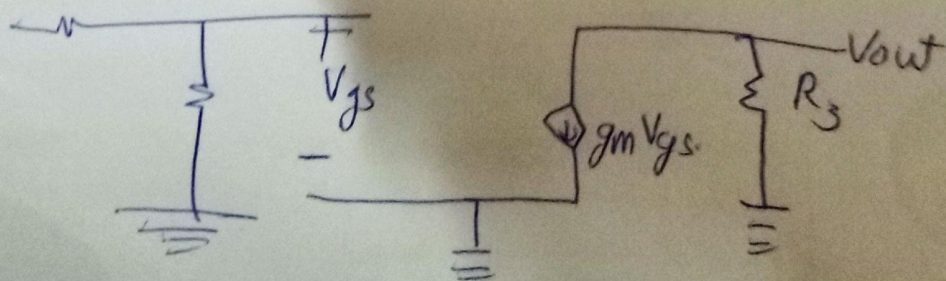



$$V_{gs} = \frac{V_{in} R_2}{R_1 + R_2} \quad \text{--- (1)}$$

Applying KCL

$$g_m V_{gs} + \frac{(V_{out} - 0)}{R_3} = 0$$

$$g_m V_{gs} = -\frac{V_{out}}{R_3}$$

we get  $g_m \left( \frac{V_{in} R_2}{R_1 + R_2} \right) = \frac{-V_o}{R_3}$

$$CL: A = \frac{V_{out}}{V_{in}} = \frac{-120 \times 10^{-3}}{1} = -0.06$$




CL gain at High frequency

$$A = -0.06$$

At very small/low freq.

Small signal equivalent

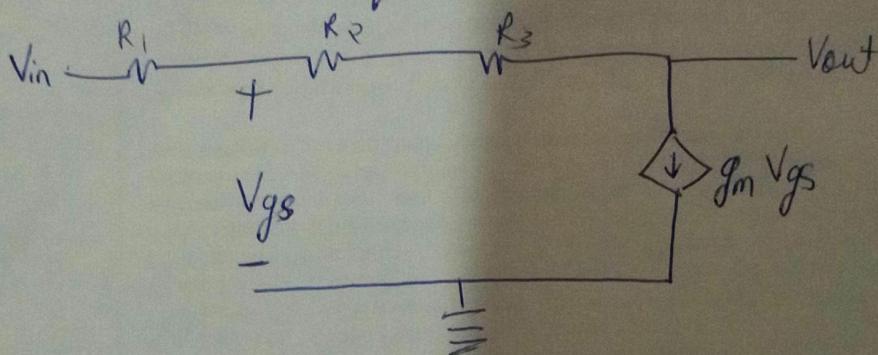

KCL at output node:

$$\frac{V_{in} - V_{out}}{R_1 + R_2 + R_3} = g_m V_{gs} \quad \text{--- (1)}$$

As same current  $g_m V_{gs}$  flows through  $R_1$ ,

$$\Rightarrow \frac{V_{in} - V_{gs}}{R_1} = g_m V_{gs}$$

$$V_{in} = (1 + g_m R_1) V_{gs}$$

$$V_{gs} = \frac{V_{in}}{1 + g_m R_1} \quad \text{--- (2)}$$

from (1) & (2)

$$\frac{V_{out}}{V_{in}} = \frac{1 - (R_1 + R_2 + R_3) g_m}{1 + g_m R_1}$$

$$= \frac{1 - 0.36}{1 + 0.628} = \frac{0.64}{1.628} = 0.394$$

CL gain at low freq

$$A = 0.628$$



2 a) negative feedback

voltage sampling  $\rightarrow$  Voltage mixing

shunt sampling  $\rightarrow$  series mixing

(b) As feedback ckt is connected in shunt with the o/p. The  $R_{out}$  for a closed loop ckt  $\downarrow$  by a factor of  $(1 + A\beta)$   $\rightarrow$  feedback factor  
 $\rightarrow$  open loop gain

$$\text{closed loop } R_{out} = \frac{\text{open loop } R_{out}}{1 + A\beta}$$

As the feedback is connected in series with the input. The i/p resistance for closed loop ckt  $\uparrow$  by factor of  $(1 + A\beta)$

$$\text{closed loop } R_{in} = (\text{open loop } R_{in}) (1 + A\beta)$$



open loop output impedance

as  $r_{ds1} = 0$  we can neglect  $r_{ds2}$  &  $r_{ds4}$

Therefore


$$\text{open loop } R_{out} = R_1 + R_2$$

OL

$$R_{out} = 2K\Omega$$

Therefore gain closed loop can be given by

$$A_v = \frac{A_o}{1 + A_o \beta}$$

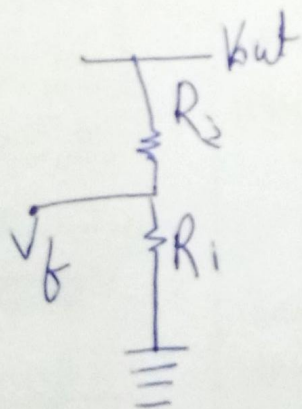

feedback factor

$$\beta = V_f / V_{out} = \frac{R_1}{R_1 + R_2}$$

$$\beta = \frac{1}{2}$$

$$\text{As } A_o = \infty$$


$$A_v = \frac{1}{\beta} = 2$$

therefore closed loop gain,

$$A_{CL} = A_v = 2$$



③ Open loop circuit.

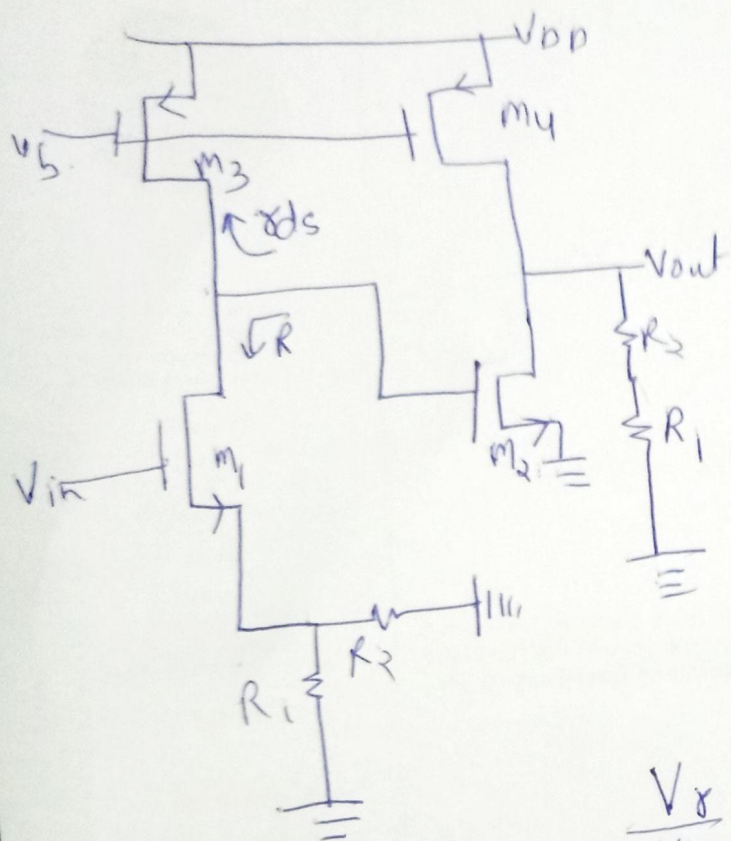

$$\text{open loop gain} = \frac{V_{out}}{V_{in}}$$

$V_{out}$  # for first stage

$$\text{gain} = \frac{V_x}{V_{in}} = -g_{m4}(r_{ds3} \parallel R)$$

$$\text{where } R = (R_1 \parallel R_2) + r_{ds1} + g_{m1}r_{ds1}(R_1 \parallel R_2)$$

$$\text{As } \lambda = 0 \Rightarrow r_{ds1} = r_{ds3} = \infty$$

$$\text{Therefore } r_{ds3} \parallel R = \infty$$

$$\frac{V_x}{V_{in}} = \infty \quad \text{--- (1)}$$

# for second stage ;  $\text{Gain} = \frac{V_{out}}{V_{in}} = -g_{m2}(R_1 + R_2)$

$$\therefore \frac{V_{out}}{V_{in}} = \left( \frac{V_x}{V_{in}} \right) \left( \frac{V_{out}}{V_x} \right) = \infty (-g_{m2}(R_1 + R_2)) = \infty$$

Therefore openloop Gain =  $\infty$

$$OL A_0 = \infty \quad \text{--- (2)}$$



closed loop output impedance  
as discussed in part B

$$CL R_{out} = \frac{OL R_{out}}{1 + A_o B}$$

as  $A_o \approx \infty$  (open loop gain)

$$\text{closed loop } R_{out} = \frac{2KR}{1 + \infty \times 1} = 0$$

Therefore closed loop  $R_{out} = 0$

$$CL \Rightarrow R_{out} = 0$$